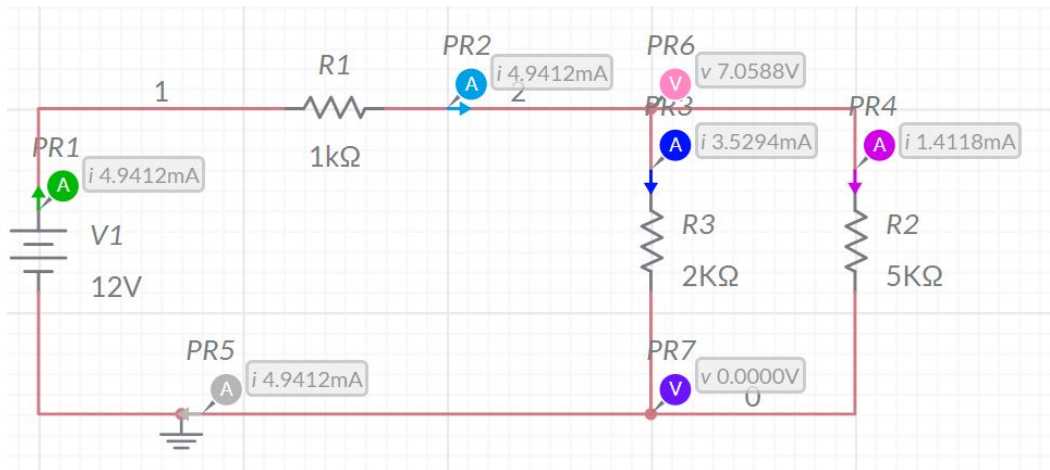


# CSU11031 Electronics Assignment 1

Róisín Ní Bhriain

18326577

1.



(i) Total Resistance of the circuit

$$R_{\text{Total}} = R_1 + R_2$$

$$\frac{1}{R_2} = \frac{1}{2} + \frac{1}{5}$$

$$= \frac{5}{10} + \frac{2}{10}$$

$$= \frac{7}{10}$$

$$\frac{1}{R_2} = \frac{7}{10}$$

$$10 = 7R_2$$

$$\frac{10}{7} = R_2$$

$$R_{\text{Total}} = \frac{10}{7} + 1$$

$$R_{\text{Total}} = \frac{17}{7} \text{ k}\Omega$$

Current

$$I = \frac{V}{R}$$

$$I = \frac{12}{\frac{17}{7}}$$

$$I = \frac{84}{17}$$

$$I = 4.9412\text{A} = PR1 = PR2 = PR5$$

Voltage at Node 2

$$PR6 = 7.0885\text{V}$$

$$V_2(t) = v(t) \left( \frac{R_2}{R + R_2} \right)$$

$$V_2 = 12 \left( \frac{\frac{10}{7}}{1 + \frac{10}{7}} \right)$$

$$V_2 = 12 \left( \frac{10}{17} \right)$$

$$V_2 = 7.0588 \text{ V}$$

# CSU11031 Electronics Assignment 1

Róisín Ní Bhriain

18326577

## Currents in parallel

$$PR3 = 3.529\text{mA}$$

$$V = IR$$

$$7.0588 = I(2)$$

$$\frac{7.0588}{2} = I$$

$$3.5294\text{mA} = I$$

$$PR4 = 1.4118\text{mA}$$

$$V = IR$$

$$7.0588 = I(5)$$

$$\frac{7.0588}{5} = I$$

$$I = 1.4118\text{mA}$$

## Voltage at PR7

$$V = IR$$

$$V = .0035294(2000)$$

$$V = 7.0588\text{V} - 7.0588\text{V}$$

$$= 0\text{V}$$

$$V = IR$$

$$V = .0014118(5000)$$

$$V = 7.0588 - 7.0588$$

$$= 0\text{V}$$

## (ii) Current Law

$$I_1 + (-I_2) + (-I_3) = 0$$

$$4.9412 - 3.5294 - 1.4118$$

$$4.9412 - 4.9412$$

$$= 0$$

## (iii) Voltage Law

$$\sum_{loop} V_{branch} = 0$$

$$E_v - V_1 - V_2 = 0$$

$$V = IR$$

$$V = 1(4.912)$$

$$= 4.912$$

$$V_1 = 4.912$$

# CSU11031 Electronics Assignment 1

Róisín Ní Bhriain

18326577




$$V_2 = 7.0588$$

$$12 - 4.9412 - 7.0588$$

$$12 - 12$$

$$= 0$$

(iv)

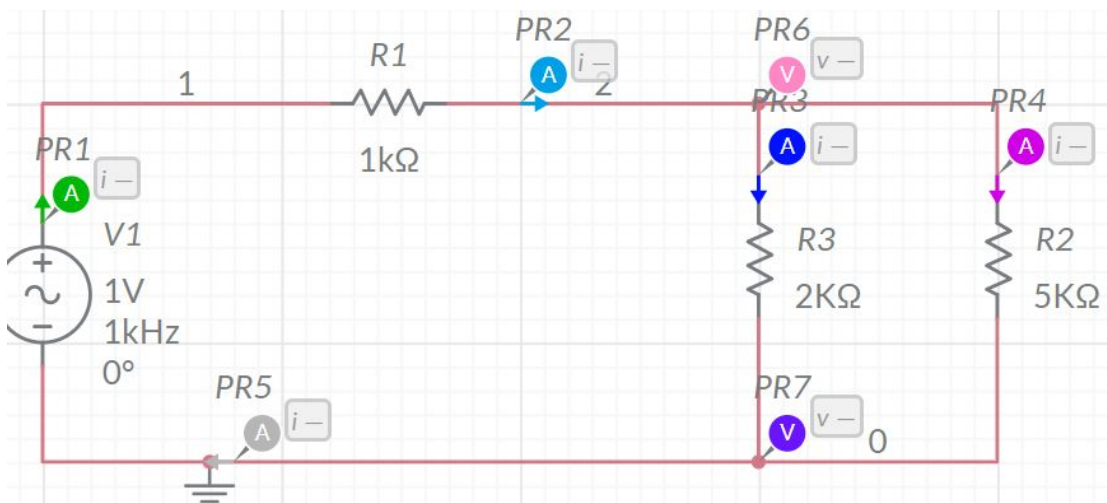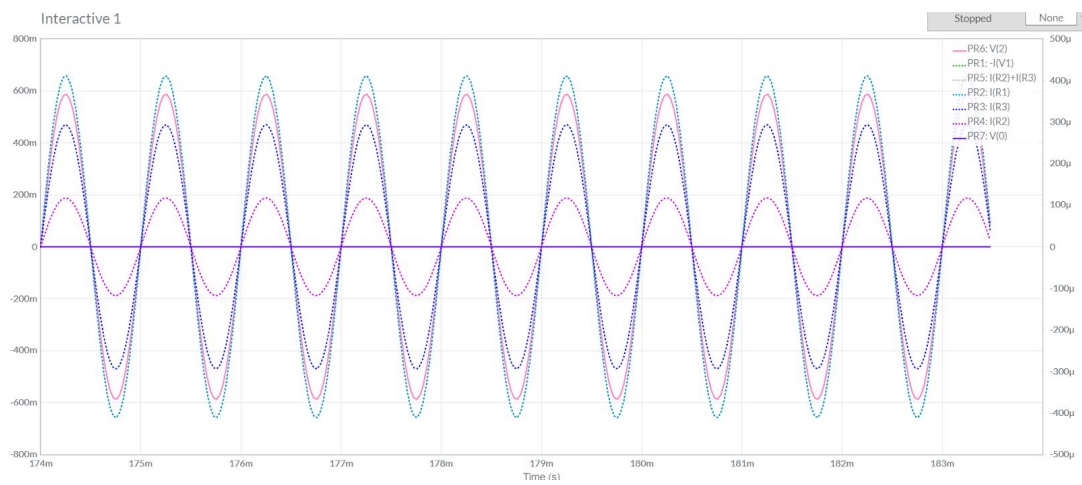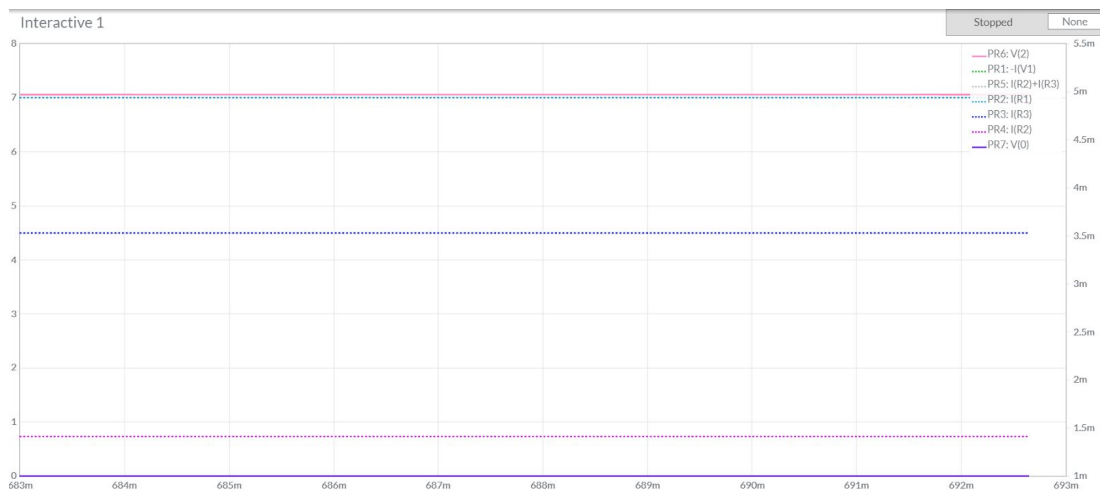

## CSU11031 Electronics Assignment 1

Róisín Ní Bhriain

18326577

The DC source has a steady output that can be observed on the graph. The AC source gives a sinusoidal output pattern due to the current changing direction.

2.

(i)



(i)

The lamp turns on as the simulation starts and shines yellow. The resistance is low so the current flowing through is high and the light is bright.

$$V1 = 40V$$

$$R1 = 80\Omega$$

$$\text{Lamp} = 10\Omega$$

$$I = \frac{40}{80+10}$$


$$I = \frac{40}{90}$$

$$I = 0.4348A$$

# CSU11031 Electronics Assignment 1


Róisín Ní Bhriain

18326577

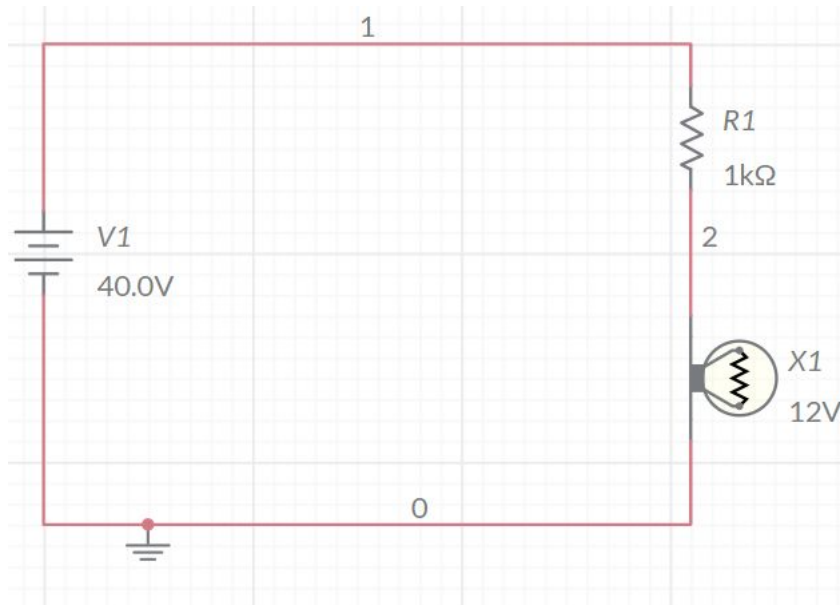

(ii)

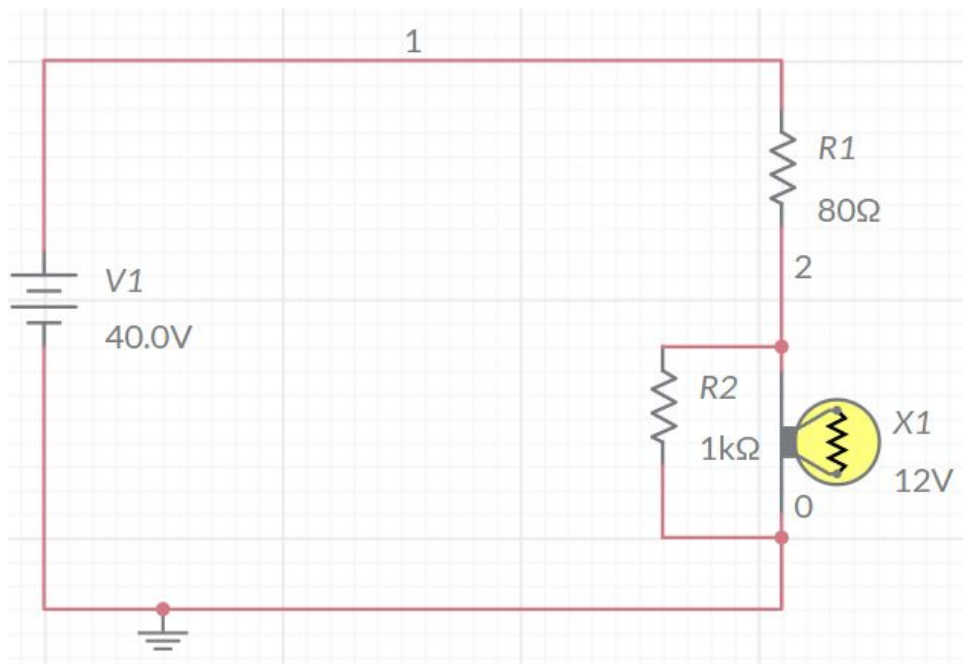The resistance is too high so the light doesn't shine.



(iii)

This time the lamp turns on.

$$V = 40V$$

$$R1 = 80\Omega$$

$$\frac{1}{R2} = \frac{1}{10} + \frac{1}{1000}$$

$$(1000) = 101R2$$

$$\frac{1000}{101} = R2$$

$$R2 = 9.90099\Omega$$

# CSU11031 Electronics Assignment 1

Róisín Ní Bhriain

18326577

$$I = \frac{V}{R_1 + R_2}$$


$$I = \frac{40}{80 + 9.90099}$$

$$I = \frac{40}{89.90099}$$

$$I = 0.44493A$$

Adding the resistors in parallel means the total resistance will decrease. Ohms law tells us that when the resistance is lower the current is higher.

(iv)

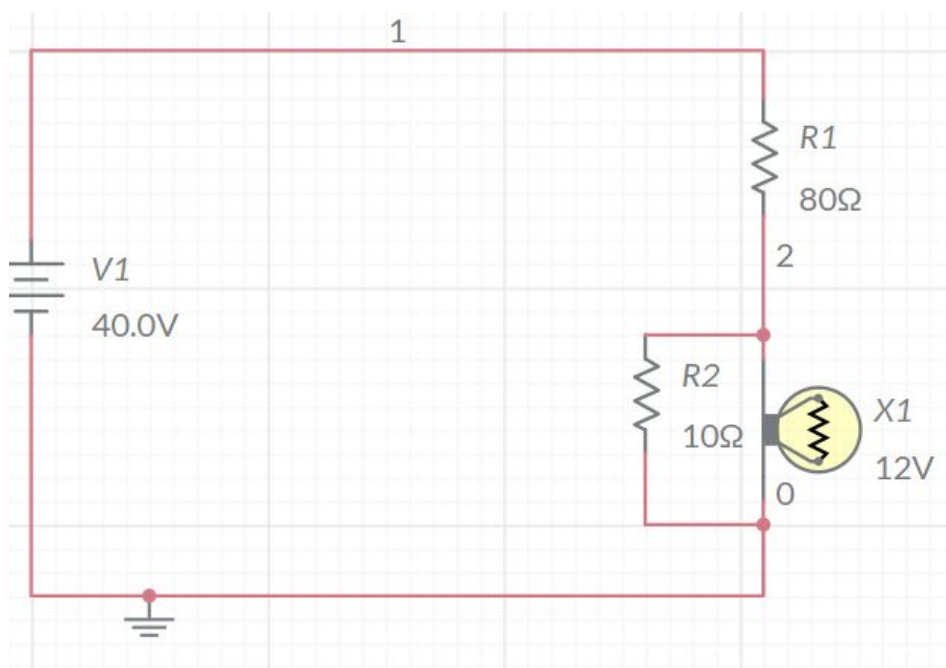

The lamp is on but with a very low light. The resistor and the lamp both have a resistance of 10Ω. Therefore the current is split between them evenly which means the current going through the lamp is halved and the light is slightly dimmer than it was previously.